

# **Birla Institute of Technology and Science Pilani Pilani Campus**



## **Assignment 1**

### **Realization of a Logic Function using CPL Logic Style**

Under the Guidance of  
Prof. Dr. Anu Gupta

Department of Electrical and Electronics Engineering  
BITS Pilani

By


**Bobba Aditya Naidu**  
**2019B4A3PS0456P**

**Kirat Bir Singh Chawla**  
**2019B1A80735P**

**Omkar R Durgada**  
**2020A3PS0460P**
 
### TASK-I

Realization of a logic function  $X = [(A \cdot B \cdot F + (B + D \cdot E \cdot F) + H)]'$  using Complementary Pass Transistor Logic Style (CPL) having load capacitance of 200fF, using a minimum number of transistors.



$$X = [(A \cdot B \cdot F + (B + D \cdot E \cdot F) + H)]'$$

Fig. 1 Design of the Boolean Expression Realization

### The Truth Table of the Expression

$$F = [(A \cdot B \cdot F + (B + D \cdot E \cdot F) + H)]'$$

a	b	d	e	f	h	Output
0	0	0	0	0	0	1
0	0	0	0	0	1	0
0	0	0	0	1	0	1
0	0	0	0	1	1	0
0	0	0	1	0	0	1
0	0	0	1	0	1	0
0	0	0	1	1	0	1
0	0	0	1	1	1	0
0	0	1	0	0	0	1
0	0	1	0	0	1	0
0	0	1	0	1	0	1
0	0	1	0	1	1	0
0	0	1	1	0	0	1
0	0	1	1	0	1	0
0	0	1	1	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	0	0
0	1	0	0	0	1	0
0	1	0	0	1	0	0

0	1	0	0	1	1	0
0	1	0	1	0	0	0
0	1	0	1	0	1	0
0	1	0	1	1	0	0
0	1	0	1	1	1	0
0	1	1	0	0	0	0
0	1	1	0	0	1	0
0	1	1	0	1	0	0
0	1	1	0	1	1	0
0	1	1	1	0	0	0
0	1	1	1	0	1	0
0	1	1	1	1	0	0
0	1	1	1	1	1	0
1	0	0	0	0	0	1
1	0	0	0	0	1	0
1	0	0	0	1	0	1
1	0	0	0	1	1	0
1	0	0	1	0	0	1
1	0	0	1	0	1	0
1	0	0	1	1	0	1
1	0	0	1	1	1	0
1	0	1	0	0	0	1
1	0	1	0	0	1	0

1	0	1	0	1	0	1
1	0	1	0	1	1	0
1	0	1	1	0	0	1
1	0	1	1	0	1	0
1	0	1	1	1	0	0
1	0	1	1	1	1	0
1	1	0	0	0	0	0
1	1	0	0	0	1	0
1	1	0	0	1	0	0
1	1	0	0	1	1	0
1	1	0	1	0	0	0
1	1	0	1	0	1	0
1	1	0	1	1	0	0
1	1	0	1	1	1	0
1	1	1	0	0	0	0
1	1	1	0	0	1	0
1	1	1	0	1	0	0
1	1	1	0	1	1	0
1	1	1	1	0	0	0
1	1	1	1	0	1	0
1	1	1	1	1	0	0
1	1	1	1	1	1	0

## Minimization

$$[(A \cdot B \cdot F + (B + D \cdot E \cdot F) + H)]'$$

$$[B \cdot (A \cdot F + 1) + D \cdot E \cdot F + H]'$$


$$[B + D \cdot E \cdot F + H]'$$

## Schematic

### Specifications:

- 
- $C_L = 1\text{pF}$ ,
- $\mu_n : \mu_p = 1.9$
- W/L for n-MOS1, 2, 3, 4, 5, 6, 7, and 8 = **8.33**


	<b>W</b>	<b>L</b>	<b>W/L</b>
<b>n-MOS</b>	1.0 $\mu\text{m}$	0.12 $\mu\text{m}$	8.33
<b>Inverter</b>	2.7 $\mu\text{m}$	0.12 $\mu\text{m}$	22.49

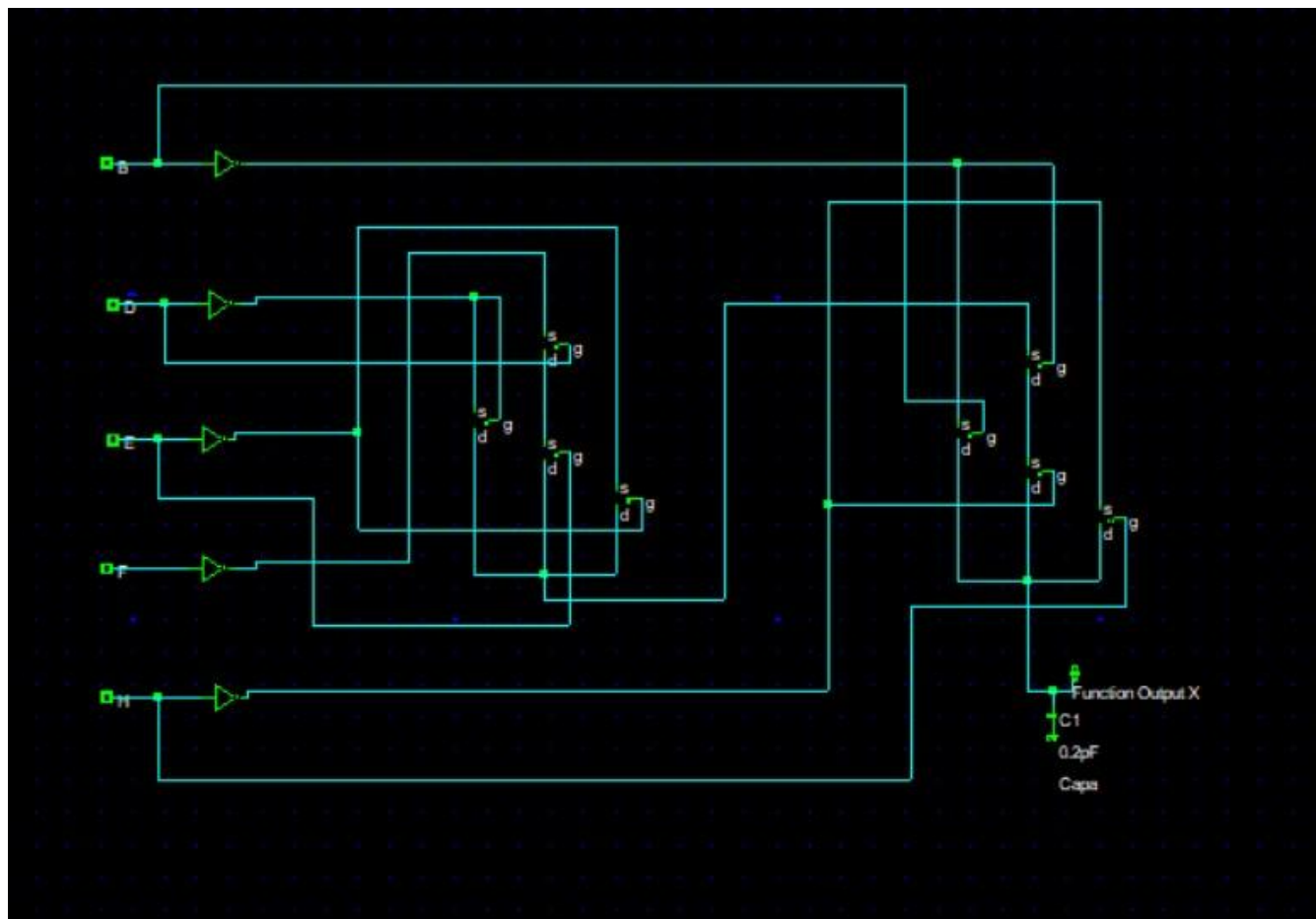

**Fig 2. Schematic of the Function**



## Design Rule Check

 

**Fig 3. DRC Verification**

## The Final Layout


 
 



Fig. 4 Microwind layout

5 lambda  
0.500um

  

 







**Fig. 5** Microwind layout (Zoomed in)

## Output



**Fig. 6 Voltage v/s Time Graph generated from Microwind**



 

**Fig. 7 Voltage v/s Time Graph generated from DSCH**

## **Innovation**

- Constructed the circuit using the DHCS tool and generated a Verilog file.
- Used the verilog file to obtain the layout for verifying the results obtained from manually designing the layout.
- Minimised the delay using logical effort ensuring that each branch of the circuit bears the same effort.

## **Problems and Challenges**

- The Microwind software being an obsolete technology is slow to use and has limited functionality.
- We have used Logical Effort in the design of our circuit, since it provides unique insight on how to minimize the delay of a circuit. However, akin to other design methodologies, there is always a tradeoff encountered between speed, power and switching capacity.
- DSCH, being an obsolete software, only supports 256 wires, symbols and Nodes which led to problems in making the schematic diagram. The schematic diagram needs to be highly optimized in order to be supported by the software.